

# Gate Assignment

Teki satyaveni

October 2023

1. Neglecting the delays due to the logic gates in the circuit shown in figure, the decimal equivalent of the binary sequence  $[ABCD]$  of initial logic states, which will not change with clock, is \_\_\_\_\_.

[EE GATE 2023]

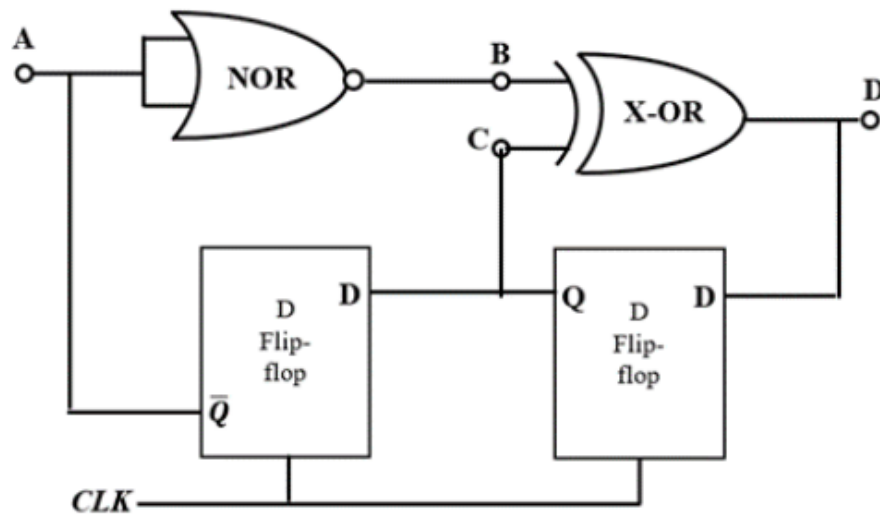


Figure 1: Neglecting the delays